

Individual Assignment -I for Section One only

1. Simplify the following Boolean function in sum-of-products and product-of sums by means of a four-variable map. Draw the logic diagram with (a) AND-OR gates; (b) NAND gates.

$$F(w, x, y, z) = \sum(2,3,4,5,6,7,11,14,15)$$

Mseries	w	x	y	z	out
M0	0	0	0	0	0
M1	0	0	0	1	0
M2	0	0	1	0	1
M3	0	0	1	1	1
M4	0	1	0	0	1
M5	0	1	0	1	1
M6	0	1	1	0	1
M7	0	1	1	1	1
M8	1	0	0	0	0
M9	1	0	0	1	0
M10	1	0	1	0	0
M11	1	0	1	1	1
M12	1	1	0	0	0
M13	1	1	0	1	0
M14	1	1	1	0	1
M15	1	1	1	1	1

		yz			
		00	01	11	10
wx	00	0	0	1	1
	01	1	1	1	1
	11	0	0	1	0
	10	0	0	1	1

SOP: $(\overline{w}x\overline{y}) + (y) + (wyz)$

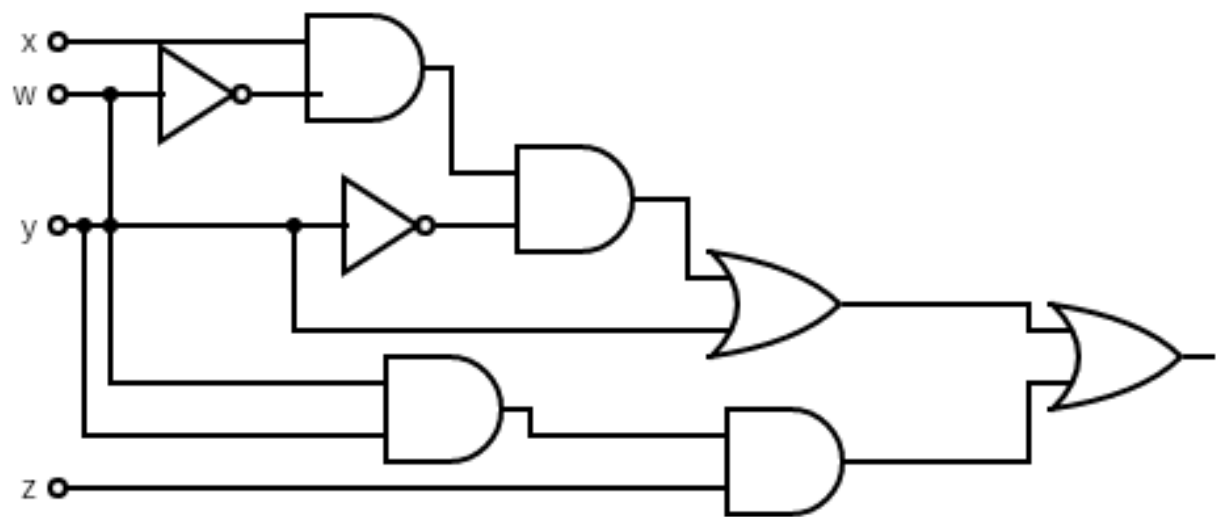


Figure 1. AND-OR for SOP

		yz			
		00	01	11	10
wx	00	0	0	1	1
	01	1	1	1	1
	11	0	0	1	0
	10	0	0	1	1

POS: $(y) * (\overline{w} + \overline{x} + z)$

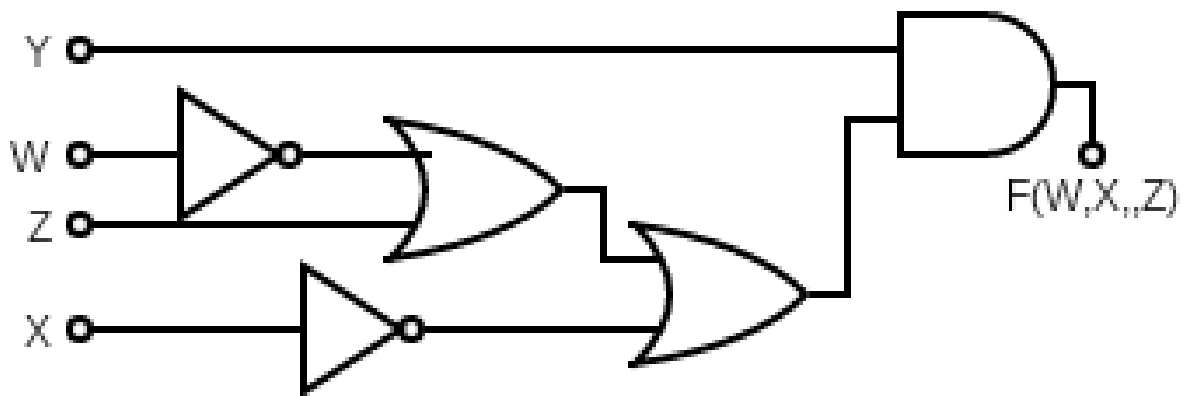


Figure 2. AND-OR for POS

2. Design a sequential circuit with two JK flip flops A and B and two inputs E and X. If $E = 0$, the circuit remains in the same state regardless of the value of x . When $E = 1$ and $X = 1$ the circuit goes through the state transitions from 00 to 01 to 10 to 11 back to 00, and repeat. When $E = 1$ and $X = 0$, the circuit goes through the state transitions from 00 to 11 to 10 to 01 back to 00, and repeat.

	Inputs		Present state		Next state		FlipFlops (Excitation)			
	E	X	A	B	A	B	JA	KA	JB	KB
Case 1	0	x	0	0	0	0	0	X	0	X
	0	x	0	1	0	1	0	X	X	0
	0	x	1	0	1	0	X	0	0	X
	0	x	1	1	1	1	X	0	X	0
Case 2	1	1	0	0	0	1	0	X	1	X
	1	1	0	1	1	0	1	X	X	1
	1	1	1	0	1	1	X	0	1	X
	1	1	1	1	0	0	X	1	X	1
Case 3	1	0	0	0	1	1	1	X	1	X
	1	0	1	1	1	0	X	0	X	1
	1	0	1	0	0	1	X	1	1	X
	1	0	0	1	0	0	0	X	X	1

K-map

A_B	JA					A_B	JB
	00	01	11	10			

EX	00	0	0	X	X
	01	0	0	X	X
	11	0	1	X	X
	10	1	0	X	X
	JA= EXB + $\overline{EX}B$				

EX	00	01	11	10	
	00	0	X	X	0
	01	0	X	X	0
	11	1	X	X	1
	10	1	X	X	1
JB=E					

EX	AB	00	01	11	10
00	X	X	0	0	
01	X	X	0	0	
11	X	X	1	0	
10	X	X	0	1	
KA=EXB+ $\overline{EX}B$					
EX	AB	00	01	11	10
00	X	0	0	X	
01	X	0	0	X	
11	X	1	1	X	
10	X	1	1	X	
KB=E					

EX	A_B	KA			
		00	01	11	10
	00	X	X	0	0
	01	X	X	0	0
	11	X	X	1	0
	10	X	X	0	1
	$KA = EXB + \overline{EX}B$				

EX	A_B	KB			
		00	01	11	10
	00	X	0	0	X
	01	X	0	0	X
	11	X	1	1	X
	10	X	1	1	X
	$KB = E$				


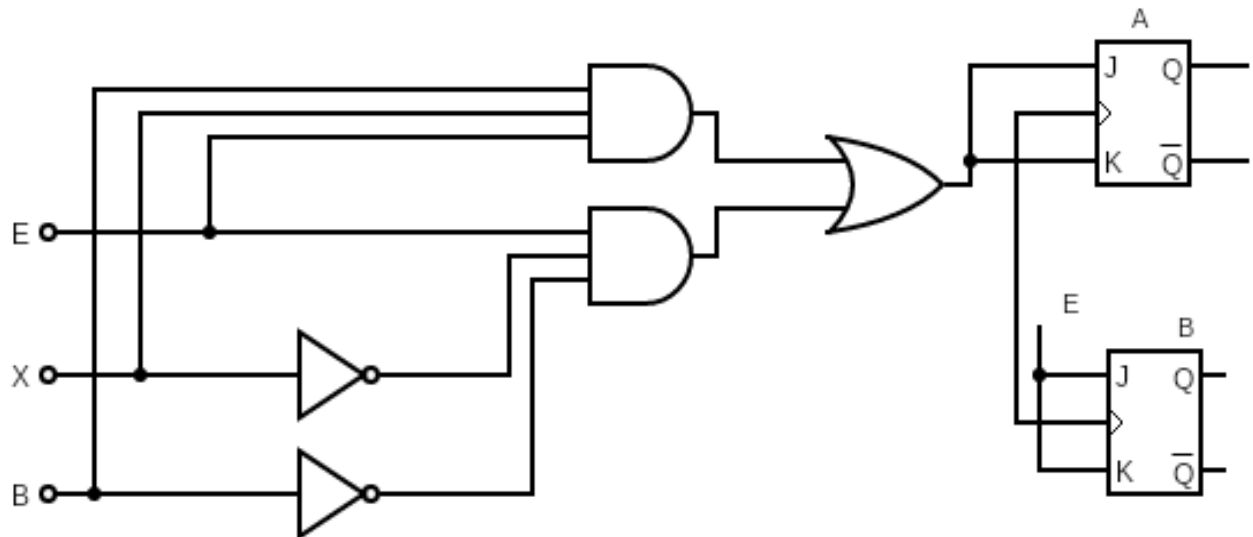


Figure 3. JK flip flop circuit

3. A counter has a special counting sequence: 0,5,7,1,0,5,7,1, and so on. Design this counter with minimal number of states.

a) Draw a state diagram for the counter

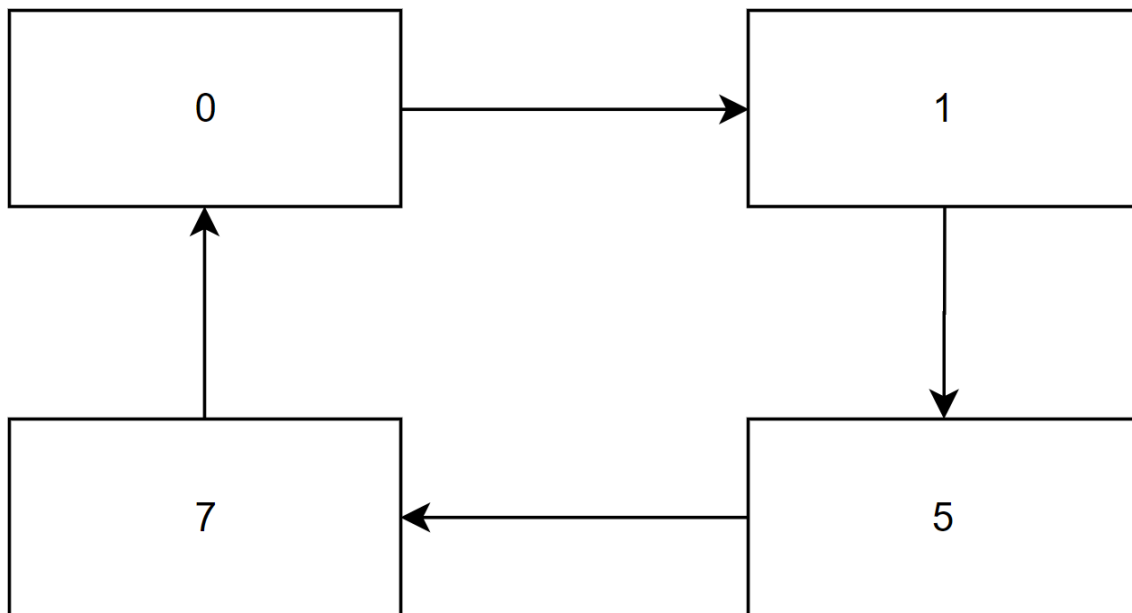

b) Construct a state-assigned table including the next state and output

Present state			Next State(state 0)		
Q2	Q1	Q0	Q2+	Q1+	Q0+
0	0	0	1	0	1
0	0	1	0	0	0
1	0	1	1	1	1
1	1	1	0	0	1

c) Draw the circuit diagram for the counter using D flip-flops

Present state			Next State					
Q2	Q1	Q0	Q2+	Q1+	Q0+	D2	D1	D0

0	0	0	1	0	1	1	0	1
1	0	1	1	1	1	1	1	1
1	1	1	0	0	1	0	0	1
0	0	1	0	0	0	0	0	0

Q1Q2

	00	01	11	10
Q0	0	1	0	0
	1	0	1	0

D2= $\overline{Q2}Q1\overline{Q0} + Q2\overline{Q1}Q0$

Q1Q2

	00	01	11	10
Q0	0	0	0	1
	1	0	0	0

D1= $Q2\overline{Q1}Q0$

Q1Q2

	00	01	11	10
Q0	0	1	0	0
	1	0	0	1

D0= $\overline{Q2}Q1\overline{Q0} + Q2Q0$

d) Repeat (c) using T flip-flops


Characteristics table

T	Q(next)
0	Q
1	Q'
$Q(\text{next}) = TQ' + T'Q$	

Present state			Next State					
Q2	Q1	Q0	Q2+	Q1+	Q0+	T2	T1	T0

0	0	0	1	0	1	1	0	1
1	0	1	1	1	1	0	1	0
1	1	1	0	0	1	1	1	0
0	0	1	0	0	0	0	0	1

<div>Q1Q2</div> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>Q0</td><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td></td><td>1</td><td>0</td><td>0</td><td>1</td></tr></table> <div>T2=Q2Q1Q0 + Q2Q1Q0</div>						00	01	11	10	Q0	0	1	0	0		1	0	0	1	<div>Q1Q2</div> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>Q0</td><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td></td><td>1</td><td>0</td><td>0</td><td>1</td></tr></table> <div>T1=Q2Q1</div>						00	01	11	10	Q0	0	0	0	1		1	0	0	1
	00	01	11	10																																			
Q0	0	1	0	0																																			
	1	0	0	1																																			
	00	01	11	10																																			
Q0	0	0	0	1																																			
	1	0	0	1																																			
<div>Q1Q2</div> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>Q0</td><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td></td><td>1</td><td>1</td><td>0</td><td>0</td></tr></table> <div>T0=Q2Q1</div>						00	01	11	10	Q0	0	1	0	0		1	1	0	0																				
	00	01	11	10																																			
Q0	0	1	0	0																																			
	1	1	0	0																																			

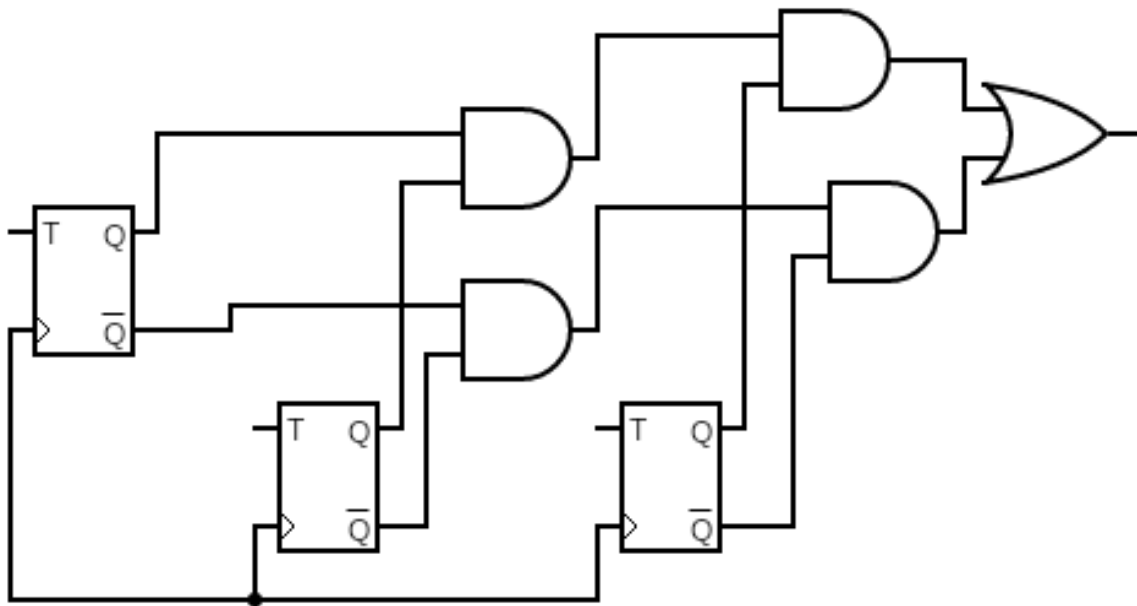

e) Repeat (c) using JK flip-flops

Present state			Next State								
Q2	Q1	Q0	Q2+	Q1+	Q0+	JQ2	KQ2	JQ1	JK1	JQ0	JK0
0	0	0	1	0	1	1	X	0	X	1	X
1	0	1	1	1	1	X	0	1	X	X	0
1	1	1	0	0	1	X	1	X	1	X	0
0	0	1	0	0	0	0	X	0	X	X	1

<div><div>Q1Q0</div><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>Q1</td><td>0</td><td>1</td><td>0</td><td></td></tr><tr><td></td><td>1</td><td></td><td>X</td><td>X</td></tr></table><div>JQ2=$\overline{Q2Q1Q0} + Q2Q1Q0$</div></div>				00	01	11	10	Q1	0	1	0			1		X	X	<div><div>Q1Q0</div><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>Q1</td><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td></td><td>1</td><td></td><td>X</td><td></td></tr></table><div>JQ1=Q2Q0</div></div>				00	01	11	10	Q1	0	0	0	1		1		X		<div><div>Q1Q0</div><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>Q1</td><td>0</td><td>1</td><td></td><td></td></tr><tr><td></td><td>1</td><td>X</td><td></td><td>X</td></tr></table><div>JQ0=$\overline{Q2Q1}$</div></div>				00	01	11	10	Q1	0	1				1	X		X
	00	01	11	10																																																	
Q1	0	1	0																																																		
	1		X	X																																																	
	00	01	11	10																																																	
Q1	0	0	0	1																																																	
	1		X																																																		
	00	01	11	10																																																	
Q1	0	1																																																			
	1	X		X																																																	
<div><div>Q1Q0</div><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>Q1</td><td>0</td><td>X</td><td>X</td><td></td></tr><tr><td></td><td>1</td><td></td><td>0</td><td>1</td></tr></table><div>JQ2=$\overline{Q2Q1Q0} + Q2Q1Q0$</div></div>				00	01	11	10	Q1	0	X	X			1		0	1	<div><div>Q1Q0</div><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>Q1</td><td>0</td><td>X</td><td>X</td><td>X</td></tr><tr><td></td><td>1</td><td></td><td></td><td>1</td></tr></table><div>KQ1=Q2Q0</div></div>				00	01	11	10	Q1	0	X	X	X		1			1	<div><div>Q1Q0</div><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>Q1</td><td>0</td><td>X</td><td></td><td></td></tr><tr><td></td><td>1</td><td>1</td><td></td><td>0</td></tr></table><div>KQ0=$\overline{Q2Q1}$</div></div>				00	01	11	10	Q1	0	X				1	1		0
	00	01	11	10																																																	
Q1	0	X	X																																																		
	1		0	1																																																	
	00	01	11	10																																																	
Q1	0	X	X	X																																																	
	1			1																																																	
	00	01	11	10																																																	
Q1	0	X																																																			
	1	1		0																																																	